



Part (2)

(35 Marks)

Answer as much as you can

[1] Question One (15 Marks):

A) The switch in Fig. (1) moves from position *A* to position *B* at $t=0$. Determine $i(t)$ for $t > 0$

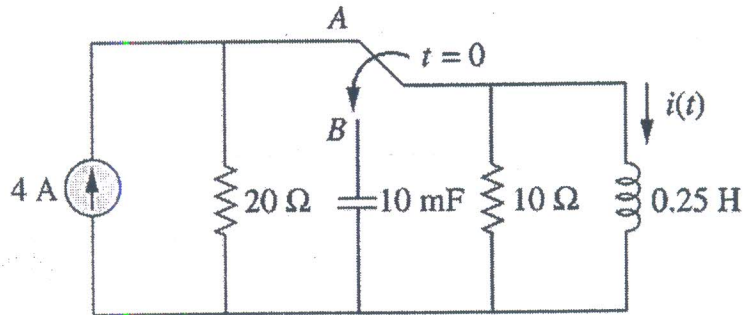


Fig. (1)

B) For the circuit in Fig. (2), if $v = 10e^{-4t}$ V and $i = 0.2e^{-4t}$ A, $t > 0$

- (a) Find *R* and *C*.
- (b) Determine the time constant.
- (c) Calculate the initial energy in the capacitor.
- (d) -Obtain the time it takes to dissipate 50 percent of the initial energy.

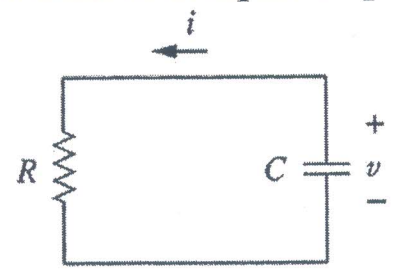


Fig. (2)

C) Find I_o in the circuit in Fig. (3)

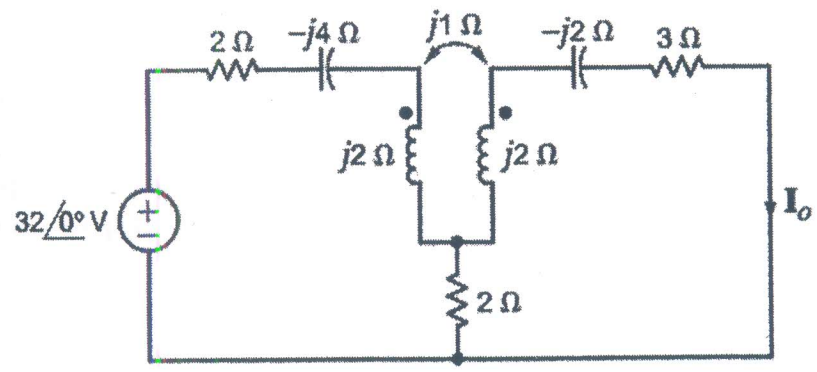


Fig. (3)