

Menoufia University
 Faculty of Electronic Engineering
 Dept. Industrial Electronics and Control Eng.
 Course: Electrical Engineering
 Course Field: Specialization Requirements
 Academic Level: First Year, 1st Semester
 Academic Year: 2019 / 2020
 Course Code: ACE 115



Final Term Exam
 Date: 16 / 1 / 2020
 Exam Type: Written - C
 No. of Exam Pages: 4
 No. of Exam Questions: 6
 Exam Marks: 60 Marks
 Exam Time: 3 Hours
 From 10:00 AM to 1:00 PM

Answer the following questions:

Part – 1:

Question – 1: Choose the correct answer for the following questions: [9 Marks]

- [1] The total charge that passes through a resistor in a period of 1.5 h, when a current of 500 mA flows is:
 a) 750 C b) 92.59 μ C c) 2700 C d) 0.75 C
- [2] An aluminum conductor has a resistance of 10 Ω at 20 $^{\circ}$ C and a temperature coefficient of 0.0039 per degree Celsius. The resistance of the conductor at 100 $^{\circ}$ C is:
 a) 6.56 Ω b) 13.12 Ω c) 131.2 Ω d) 26.24 Ω
- [3] A current of 100 mA is supplied from a battery until a charge of 350 C is taken from the battery. The time for which the current must flow is:
 a) 3.5 sec b) 58.33 min c) 41.66 min d) 9.72 hours
- [4] Suppose a power amplifier delivers 400 W to its speaker system. If the power loss is 509 W, then its efficiency is:
 a) 78.58% b) 44% c) 127.25% d) 88.71%
- [5] An electric heater takes a current of 15 A when connected to a 120 V supply. The conductance of the heater is:
 a) 0.1 S b) 0.08 S c) 0.125 S d) 0.75 S
- [6] A motor drives a pump through a gearbox as depicted in Figure 1. Power input to the motor is 1200 W. The output of the gearbox (and hence the input to the pump) is:
 a) 1920 W b) 192 kW c) 756 W d) 7.56 MW

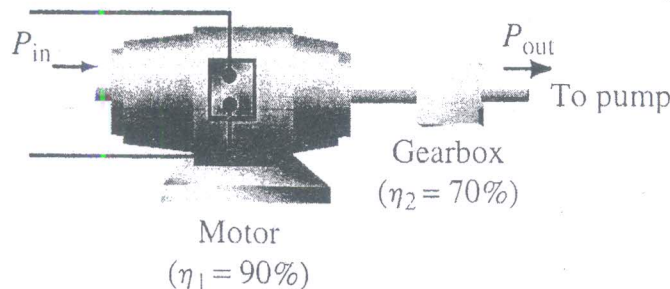


Figure 1

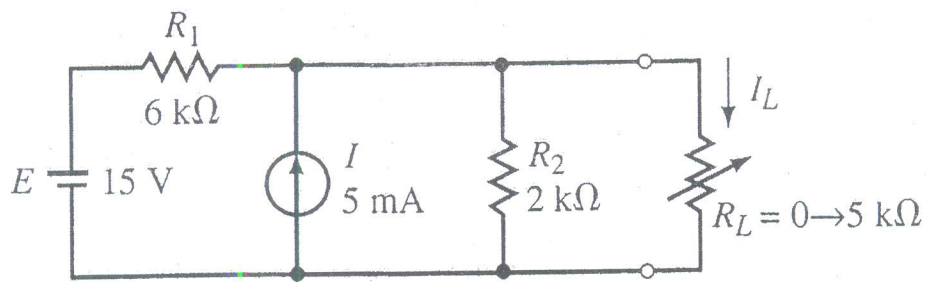


Figure 3

[9 Marks]

Part – 2:

Question – 4: For the ac circuit shown in Figure 4, the capacitor is of $C = 250 \mu\text{F}$ and the shown coil part impedance is given as $10 + j 31.4 \Omega$. If the ac input voltage is given as $V_s = 7 \sin(100\pi t)$,

- Calculate the circuit current
- Calculate the voltage V_R , V_L and V_C
- Determine the power factor
- Find the resonance frequency
- Draw the phasor diagram for the circuit
- Sketch the relation between the circuit impedance Z versus the frequency f
- If the coil is considered a pure conductance, determine the value of the average power at resonance frequency.

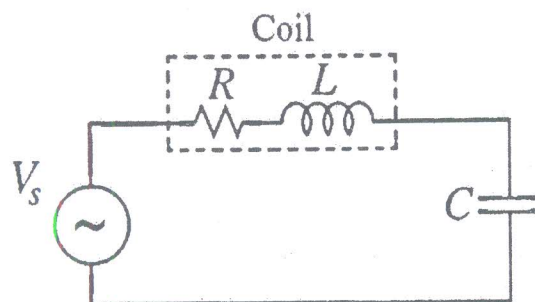


Figure 4

[10 Marks]

Question – 5: A generator supplies power to an electric heater, an inductive element, and a capacitor as in the ac circuit shown in Figure 5,

- Find P and Q for each load.
- Find P_T and Q_T supplied by the generator.
- Draw the power triangle for the combined loads.
- Find the current supplied by the generator.

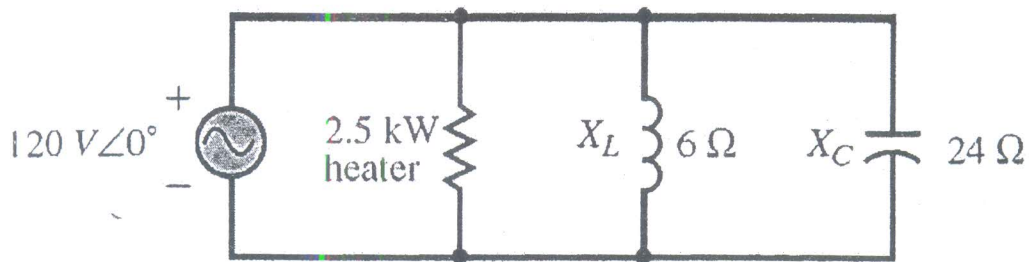


Figure 5

[10 Marks]

Question – 6:

a) Sketch the instantaneous sinusoidal waveforms of voltage V , current I and power P for:

- i. A purely resistive circuit.
- ii. A purely inductive circuit.
- iii. A purely capacitive circuit.

[3 Marks]

b) For the circuit shown in Figure 6, if the supply voltage is given as $V_s = 117 \sin(120\pi t)$, Calculate the complex power and correct the power factor to be unity.

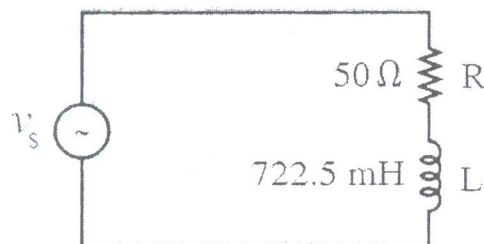


Figure 6

[7 Marks]

With best wishes